

Contents

1	Between the Transistor and the High-Level Language	1
1.1	Prior Perceptions	1
1.2	A Spectrum of Digital Languages	3
1.3	Control Flow	6
1.4	Terms and Roles	8
1.5	Some Digital History	9
2	Boolean Algebra and Digital Logic	11
2.1	Computer Logic Circuits	11
2.2	Application of Logic Circuits	15
2.3	Evaluation of Boolean Functions	19
2.4	Boolean Algebra	21
2.5	Simplification of Boolean Functions	26
2.6	Boolean Algebra as an Algebra of Subsets	28
2.7	On the History of the Algebra of Logic	31
	Problems	31
	References	33
3	0, 1: Binary Numbers or Logical Values?	35
3.1	The Binary Number System	35
3.2	Conversion between Bases	37

3.3	Binary Coding of Decimal Digits	40
3.4	Historical Note	43
	Problems	44
	References	44
4	Simplification of Boolean Functions	45
4.1	Standard Forms of Boolean Functions	45
4.2	Karnaugh Map Representation of Boolean Functions	52
4.3	Simplification of Functions on the Karnaugh Map	60
4.4	Map Minimization of Product-of-Sums Expressions	66
4.5	Incompletely Specified Functions	68
	Problems	71
	References	73
5	Standard Digital Integrated Circuits	75
5.1	Introduction	75
5.2	Small-Scale Integrated Circuits	79
5.3	Fan-out, Fan-in, and Noise Immunity	80
5.4	Switching Delay in Logic Circuits	85
5.5	Circuit Implementation with NAND and NOR Gates	87
5.6	Multilevel All-NAND Realizations	89
5.7	Reducing Package Counts in Multilevel Realizations	94
	Problems	98
	References	101
6	Computer Arithmetic and Codes	101
6.1	Introduction	103
6.2	Conversion between Number Bases	103
6.3	Coding of Information	106
6.4	Parity	111
6.5	Binary Arithmetic	113
6.6	Implementation of Binary and BCD Addition	117
6.7	Carry and Overflow	121
	Problems	123
	References	126
7	Combinational MSI Parts, ROMs, and PLAs	127
7.1	Perspective	127
7.2	Combinational MSI Parts	128
7.3	Read-Only Memory	137
7.4	Chip-Select, Buses, and Three-State Switches	144

7.5	Programmed Logic Arrays	147
7.6	Describing Multiplexers with a Graphic Vector Notation	153
7.7	Special Purpose MSI Parts	154
	Problems	158
	References	161
8	Sequential Circuits	163
8.1	Storage of Information	163
8.2	Clocking	166
8.3	Registers	171
8.4	Memory Element Input Logic	173
8.5	A First Design Example	174
8.6	The <i>J-K</i> Flip-Flop	177
8.7	Design of Counters	181
8.8	MSI Registers and Counters	187
	Problems	195
	References	197
9	Synthesis of State Machines	199
9.1	A Language is Needed	199
9.2	Standard Symbols for the ASM Chart	200
9.3	Vending Machine Control	204
9.4	From ASM Charts to Transition Tables	208
9.5	Circuit Realization	212
9.6	The State Diagram, an Alternative Notation	216
9.7	Compatible States	221
	Problems	223
	References	227
10	Register Transfer Design	229
10.1	Generalized ASM Output	229
10.2	ASM Chart Representation of a Control Unit	231
10.3	Register Transfer Language (RTL) Notation	233
10.4	Construction of a Data Unit from an RTL Description	239
10.5	Timing of Connections and Transfers	242
10.6	Sequencing of Control	245
10.7	Combinational Logic and Conditional Transfers	248
10.8	Graphical and RTL Bus Notation	254
10.9	Timing Refinements in RTL Systems	256
10.10	An RTL Design Example	257
	Problems	262
	References	266

11	Small Computer Organization and Programming	267
11.1	Introduction	267
11.2	Central Processor and Memory Organization	268
11.3	CPU Organization and Instruction Formats	270
11.4	Fundamental Internal Sequence of a Single-Address Computer	272
11.5	Transfer-of-Control and Register-Only Instructions	279
11.6	Addition and Subtraction with Carry	286
11.7	Commands That Affect Only the Flags	290
11.8	Programming Procedures	292
	Problems	296
12	Addressing and Assembly Language	301
12.1	Microprocessor Addressing	301
12.2	Addressing Modes	302
12.3	Assembly Language Programming	311
12.4	More Programming	316
12.5	Data Conversion, Decimal Arithmetic, and Subroutines	320
	Problems	330
13	Memory and Input/Output	333
13.1	Memory Mapping	333
13.2	Timing of Memory Operation	338
13.3	Parallel Input/Output Interfacing	340
13.4	Interactive Input/Output	346
13.5	Programming Time Delays	355
13.6	Device Drivers	359
13.7	Substituting Input Scanning for Combinational Logic	366
13.8	Time-Sharing of Interface Ports	370
	Problems	375
	References	378
14	Serial Input/Output	379
14.1	Serial to Parallel Conversion	379
14.2	A Serial Communications Interface Adapter TBSIA	388
14.3	A Subroutine for Serial I/O through a TBSIA	393
14.4	Interconnecting RS-232 Equipments	396
14.5	Computer Networks	400
	Problems	403
	References	406

15	Additional Programming Topics	407
15.1	Pointer Addressing and Stacks	407
15.2	Subroutines	411
15.3	Interrupts	426
15.4	Start-up and Reset	437
15.5	Tables and Other Data Structures	439
	Problems	450
	References	455
16	Microprocessor-Based Systems Design	457
16.1	Introduction	457
16.2	Vending Machine Operation	457
16.3	System Specifications	459
16.4	Control Unit Design	462
16.5	Planning the Program	465
16.6	Memory Map Layout	471
16.7	Coding the Program	475
	Problems	479
17	The Clock-Mode Assumption Reexamined	481
17.1	Attention to Output Waveforms	481
17.2	Elimination of Hazards	484
17.3	Synchronizing Inputs to Clock-Mode Circuits	486
17.4	Clock Skew on Edge-Triggered Flip-Flops	491
17.5	Is That Clock Really Necessary?	493
17.6	Synthesis of Level-Mode Sequential Circuits from a Flow Table	498
17.7	Races in State Variable Transitions	504
17.8	Critical Race-Free State Assignments	511
17.9	More Constraints on Level-Mode Realizations	516
	Problems	518
	References	522
Appendix A	Powers of Two	523
Appendix B	Summary of TB6502 Instruction Set	524
Appendix C	TB6502 Instruction Set: Opcodes, Bytes, Cycles	527
Appendix D	Mapping the TB6502 into the 6502	530
Index		533