

CONTENTS

- 1. Introduction, 5**
 - 1.1 Concept of an electric circuit, 5
 - 1.2 Charge, current, Kirchhoff's current law, 6
 - 1.3 Voltage, power, Kirchhoff's voltage law, 7
 - 1.4 Time functions of circuit variables, 8
- 2. Circuit elements, 11**
 - 2.1 Classification, 11
 - 2.2 Basic active elements, 12
 - 2.3 Basic passive elements, 13
 - 2.4 Basic rules of equivalence, 16
- 3. Resistive circuits, 18**
 - 3.1 Elementary analysis, 18
 - 3.2 Thevenin's and Norton's theorems, 20
 - 3.3 Superposition theorem, 23
 - 3.4 Power and power matching, 23
- 4. Circuit equations, 25**
 - 4.1 Topology of electric circuits, 25
 - 4.2 Independent circuit equations, 27
 - 4.3 Direct application of the KCL and KVL, 28
 - 4.4 Loop current analysis, 29
 - 4.5 Nodal voltage analysis, 31
 - 4.6 Reciprocity theorem, 33
- 5. Sinusoidal steady state, 35**
 - 5.1 Sinusoidal function, 35
 - 5.2 Basic circuit elements at the sinusoidal excitation, 35
 - 5.3 Phasors, 37
 - 5.4 Impedance and admittance, 39
 - 5.5 Rules of equivalence, elementary circuit analysis, 41
 - 5.6 Phasor diagrams, 44
 - 5.7 Circuit theorems for the sinusoidal steady state, 46
 - 5.8 Power and power matching, 48
 - 5.9 Circuit equations for the sinusoidal steady state, 50
 - 5.10 Circuit functions, 56
 - 5.11 Frequency characteristics, 58
 - 5.12 Resonant circuits, 65
 - 5.13 Three-phase systems, 69
- 6. Transients, 75**
 - 6.1 Circuit equations for transients, 75
 - 6.2 First order circuits, 76
 - 6.3 Higher order circuits, 86
- 7. Recommended books, 93**