

Contents:

1. Exercise and problem solving

1.1. Non-linear Circuits.....	5
1.2. Transients.....	26
1.3. Operational analysis.....	44
1.4. Two-ports.....	61
1.5. Feedback circuits.....	74
1.6. Generalized Nodal Voltage Methods.....	88
1.7. Transmission Lines.....	98

2. Laboratory exercises

2.1. DC voltage stabilizer.....	111
2.2. Superposition and modulation.....	112
2.3. Transients in RL circuits.....	114
2.4. Transients in RC circuits.....	117
2.5. Transients in RLC circuit.....	120
2.6. Transient responses.....	122
2.7. Two-ports.....	124
2.8. Transients on a lossless transmission line.....	125
2.9. Sinusoidal steady state on a lossless transmission line.....	127

3. Homeworks

3.1. Numerical analysis of non-linear circuits.....	129
3.2. Circuits with operational amplifiers.....	131
3.3. Generalized nodal voltage analysis.....	133
3.4. Sinusoidal steady state on a homogeneous transmission line.....	136

4. Answers to problems.....

137

5. References.....

171