

# CONTENTS

Contents .....	3
Preface .....	6
List of symbols .....	8
<b>1. Basic concepts</b> .....	11
1.1 Electrical devices and circuits .....	11
1.2 Models .....	13
1.3 Analysis and synthesis .....	14
1.4 Classification of circuits .....	14
1.5 Basic quantities, laws and parameters .....	16
<b>2. Circuit variables</b> .....	23
2.1 Classification of time functions .....	23
2.2 Stationary and periodic variables .....	24
2.3 Non-periodic variables .....	29
<b>3. Circuit elements</b> .....	31
3.1 Classification of elements .....	31
3.2 Resistor .....	33
3.3 Inductor .....	39
3.4 Capacitor .....	48
3.5 Basic active two-terminals .....	53
3.6 Equivalence of passive two-terminals .....	56
3.7 Equivalence of active two-terminals .....	64
<b>4. Resistive circuits</b> .....	69
4.1 Elements of resistive circuits .....	69
4.2 Power and power matching .....	75
4.3 Elementary analysis of linear circuits .....	78
4.4 Analysis of non-linear resistive circuits .....	84
4.5 Approximation of non-linear characteristics .....	85
4.6 Analytical methods .....	90
4.7 Graphical methods .....	93
4.8 Numerical methods .....	98

<b>5. Circuit equations</b> .....	105
5.1 Topology of electrical circuits .....	105
5.2 Independent circuit equations .....	109
5.3 Direct application of Kirchhoff's laws .....	110
5.4 Loop analysis .....	112
5.5 Nodal analysis .....	116
5.6 Cut-set analysis .....	121
5.7 Solution of circuit equations .....	123
<b>6. Basic transients</b> .....	125
6.1 Basic concepts .....	125
6.2 First order circuits .....	128
6.3 Second order circuits .....	140
<b>7. Sinusoidal steady state</b> .....	149
7.1 Sinusoidal variables .....	149
7.2 Phasors .....	152
7.3 Basic passive two-terminals at sinusoidal excitation .....	156
7.4 Network functions .....	159
7.5 Power .....	168
7.6 Elementary analysis .....	174
7.7 Circuit equations for sinusoidal steady state .....	181
7.8 Effects of circuit parameter variation .....	188
7.9 Frequency response .....	191
7.10 Resonance .....	201
7.11 Three-phase systems .....	208
<b>8. Periodic steady state</b> .....	216
8.1 Fourier series .....	216
8.2 Effective value and distortion factor .....	222
8.3 Power of periodic voltages and currents .....	224
8.4 Periodic steady state in linear circuits .....	227
8.5 Effects of non-linearities on frequency spectra .....	232

---

<b>9. Operational analysis</b> . . . . .	237
9.1 The Fourier transform . . . . .	237
9.2 The Laplace transform . . . . .	243
9.3 Operational characteristics . . . . .	245
9.4 Operational circuit equations . . . . .	248
9.5 Network theorems . . . . .	250
<b>10. Transfer characteristics</b> . . . . .	253
10.1 The unit impulse response . . . . .	253
10.2 The unit step response . . . . .	255
10.3 Convolution . . . . .	256
<b>11. Multi-terminal element circuits</b> . . . . .	261
11.1 Two-port characteristics . . . . .	261
11.2 Transfer properties . . . . .	269
11.3 Two-port connections . . . . .	274
11.4 Basic two-ports . . . . .	277
11.5 Feedback circuits . . . . .	281
11.6 Analysis of circuits with $n$ -terminals . . . . .	295
<b>12. Distributed circuits</b> . . . . .	301
12.1 Parameters and basic equations . . . . .	301
12.2 Lossless line . . . . .	303
12.3 Wave equations for the sinusoidal steady state . . . . .	311
12.4 Line of finite length . . . . .	317
12.5 Reflection coefficient and standing waves . . . . .	321
12.6 Wave frequency spectra . . . . .	326
<b>Appendices</b> . . . . .	329
<b>Bibliography</b> . . . . .	332