

Content

1. Introduction	11
2. Operational amplifiers.....	13
2.1 Parameters of operational amplifiers	13
2.1.1 Static parameters of operational amplifiers	13
2.1.2 Dynamic parameters of operational amplifiers	15
2.1.3 Noise parameters of operational amplifiers	16
2.2 Types of operational amplifiers	19
2.2.1 Bipolar operational amplifiers.....	19
2.2.2 Unipolar operational amplifiers.....	22
2.2.3 Frequency characteristic correction of operational amplifiers	24
2.2.4 Transconductance operational amplifiers	26
2.2.5 Transimpedance operational amplifiers	27
2.2.6 Auto-zeroed operational amplifiers	28
2.2.7 Overview of typical operational amplifiers	29
2.3 Feedback connections of operational amplifiers	31
2.3.1 Negative feedback	31
2.3.2 Static properties of negative feedback amplifiers	31
2.3.3 Dynamic properties of negative feedback amplifiers	34
2.3.4 Frequency stability of negative feedback operational amplifiers	37
2.3.5 Noise properties of negative feedback operational amplifiers.....	39
3. Linear signal processing	41
3.1 Asymmetric voltage amplifiers	41
3.1.1 Basic properties of voltage amplifiers.....	41
3.1.2 Frequency compensation of voltage amplifiers	44
3.1.3 Input impedance in voltage amplifiers	44
3.2 Current amplifiers	47
3.2.1 Properties of current amplifiers	47
3.2.2 Current amplifier with resistor T-network.....	49
3.2.3 Frequency compensation of current amplifiers	50
3.2.4 Noise in current amplifiers	52
3.3 Differential amplifiers	52
3.3.1 Differential amplifiers with asymmetric output	52
3.3.2 Signal operations with differential amplifiers	55
3.3.3 Differential amplifiers with differential voltage outputs	57
3.4 Instrumentation amplifiers	59
3.4.1 Asymmetric instrumentation voltage amplifiers	59
3.4.2 Symmetric instrumentation voltage amplifiers	61
3.4.3 Instrumentation amplifiers with switchable gain.....	64
3.4.4 Instrumentation amplifiers with current output.....	66
3.5 Integration and charge amplifiers.....	67
3.5.1 Inverting integration amplifiers	67
3.5.2 Summing and differential integration amplifiers	70
3.5.3 Charge amplifiers.....	71

3.6	Sampling amplifiers	73
3.6.1	Direct coupled sampling amplifiers.....	73
3.6.2	Feedback sampling amplifiers.....	75
3.7	Amplifiers of resistance and reactance sensors.....	76
3.7.1	Potentiometric sensor amplifiers	76
3.7.2	Strain gauge amplifiers	77
3.7.3	Capacitive sensor amplifiers	79
3.7.4	Amplifiers in measuring circuit for inductance sensors	82
3.8	Temperature sensor amplifiers	85
3.8.1	Resistance temperature sensor amplifiers	85
3.8.2	Linearization of resistance temperature sensors	87
3.8.3	PTC and NTC temperature sensor amplifiers	88
3.8.4	Semiconductor temperature sensor amplifiers	90
3.8.5	Amplifiers for thermocouples.....	93
3.9	Isolation amplifiers.....	96
3.9.1	Isolation amplifier properties	96
3.9.2	Isolation amplifiers with transformer coupling.....	97
3.9.3	Isolation amplifiers with capacitive coupling	98
3.9.4	Modulating isolation amplifiers with optical coupling	99
3.9.5	Directly optically coupled isolation amplifiers	100
4.	Non-linear signal processing	102
4.1	Comparators	102
4.1.1	Comparators types	102
4.1.2	Voltage comparators with hysteresis.....	103
4.1.3	Comparators with adjustable hysteresis.....	106
4.1.4	Window comparators	107
4.2	Function approximation circuits	107
4.2.1	Piecewise-function approximation circuits	107
4.2.2	Circuits with continuous approximation of a function	112
4.3	Analog multipliers and dividers	115
4.3.1	Multipliers properties.....	116
4.3.2	Transconductance multipliers	116
4.3.3	Logarithmic multipliers	118
4.3.4	Modulation multipliers	119
4.4	Mean value converters	120
4.4.1	Non-controlled rectifiers	120
4.4.2	Controlled rectifiers	123
4.5	RMS converters.....	125
4.5.1	Thermal RMS converters	126
4.5.2	Logarithmic RMS converters	127
4.6	Peak and peak-to-peak values detectors	128
4.6.1	Peak detectors	128
4.6.2	Peak-to-peak detectors	130
5.	Analog signal filtering	131
5.1	Types of analog filters	131
5.2	Approximation of frequency characteristics	133

5.3	Passive filters	135
5.3.1	Passive RC filters	135
5.3.2	Passive LR filters	137
5.4	Active filters	139
5.4.1	Active LP and HP filters of the 1st order.....	139
5.4.2	Active LP and HP 2nd order filters	140
5.4.3	Active HP and LP filters higher order	142
5.4.4	Active BP and BS filters of the 2nd order	143
5.4.5	All pass filters.....	145
5.4.6	Universal filters	146
5.5	Switched capacitor filters	148
6.	Switching and multiplexing of analog signals.....	150
6.1	Signal switches.....	150
6.1.1	Contact switches.....	150
6.1.2	Diode switches.....	150
6.1.3	Switches with bipolar transistors	152
6.1.4	Switches with unipolar transistors	154
6.1.5	CMOS switches	155
6.2	Analog multiplexers	156
7.	Voltage and current references	160
7.1	Voltage reference	160
7.1.1	Voltage references with Zener diodes	160
7.1.2	Voltage references with bipolar transistors.....	162
7.1.3	Voltage references with unipolar transistors.....	163
7.2	Current sources	164
7.2.1	Current sources with ungrounded load	164
7.2.2	Current sources with grounded load	164
8.	Signal digitization and reconstruction	167
8.1	Sampling of continuous signals	167
8.1.1	Equidistant sampling	167
8.1.2	Band pass sampling	168
8.1.3	Equivalent sampling	170
8.1.4	Random sampling	170
8.1.5	Adaptive sampling	171
8.2	Quantization of signals	171
8.2.1	Quantization of harmonic signals	171
8.2.2	Signal-to-noise ratio of quantized harmonic signals	173
8.2.3	Uncertainty of sampling time and quantizing signals	175
8.3	Methods of increasing the resolution of quantizes	176
8.3.1	Increase the resolution by oversampling	176
8.3.2	Increasing the resolution by dithering.....	177
8.4	Signal coding	179
8.4.1	Binary coding	179
8.4.2	BCD coding	180

8.5	Reconstruction of quantized signals	181
8.5.1	Signal reconstruction by stepped interpolation	181
8.5.2	Signal reconstruction by linear interpolation	183
8.5.3	Reconstruction of the signal by higher order polynomials	184
8.5.4	Harmonic signal reconstruction	185
9.	Analogue to Digital Conversion	187
9.1	Parameters of ADCs.....	187
9.1.1	Static parameters of ADCs.....	187
9.1.2	Dynamic parameters of ADCs.....	188
9.1.3	Noise parameters of ADCs	190
9.2	High speed ADCs.....	191
9.2.1	Parallel ADCs	191
9.2.2	Propagation ADCs	193
9.3	Feedback ADCs	195
9.3.1	Approximation ADCs.....	195
9.3.2	Tracking ADCs.....	197
9.4	Integrating ADCs	198
9.4.1	Voltage-to-frequency converters	198
9.4.2	Single slope integrating ADCs	200
9.4.3	Dual slope integrating ADCs	201
9.4.4	Triple slope integrating ADCs	202
9.4.5	Quad slope integration ADCs.....	204
9.4.6	Series mode rejection by integration ADCs.....	205
9.5	Delta sigma ADCs	207
9.5.1	Delta sigma modulation	207
9.5.2	Noise suppression by delta sigma modulators	210
9.5.3	Circuit solution of delta sigma modulators.....	211
9.5.4	Digital filters in delta sigma ADCs	214
9.6	Data acquisition systems	218
9.6.1	Parallel data acquisition systems	218
9.6.2	Multiplexing data acquisition systems	218
9.6.3	Error correction of in data acquisition systems	222
10.	Digital to Analogue Conversion	223
10.1	Parameters of DACs.....	223
10.1.1	Static parameters of DACs.....	223
10.1.2	Dynamic parameters of DACs.....	224
10.1.3	Noise parameters of DACs	224
10.2	Parallel DACs	224
10.2.1	DACs converters with switched resistor networks	224
10.2.2	DACs with switched current sources	228
10.2.3	Multiplying DACs	230
10.2.4	Switching capacitors DACs	231
10.3	Modulation DACs	231
10.3.1	Pulse width modulation DACs	232
10.3.2	Delta sigma DACs	234

11. Signal generation	236
11.1 Analog signal generators	236
11.1.1 Sinewave oscillators	236
11.1.2 Function generators	240
11.1.3 Crystal controlled oscillators (XTAL oscillators).....	242
11.1.4 Analog noise generators	244
11.2 Digitally controlled generators	246
11.2.1 Generators of deterministic signals with DDS	246
11.2.2 Pseudo-random signals generators	248
11.3 Phase synchronization and frequency synthesis	249
11.3.1 Phase synchronization circuits.....	249
11.3.2 Frequency synthesis.....	254
12. Testing of digitizers.....	256
12.1 Critical parameters of digitizers	256
12.2 Testing of static parameters	256
12.3 Testing of dynamic properties of digitizers	257
12.3.1 Sine wave fit tests	258
12.3.2 Spectral analysis methods	260
12.3.3 Histogram tests.....	266
12.3.4 Noise histogram tests	269
13. Design of data acquisition systems	272
13.1 Long distance signal transmission	272
13.2 Connecting of amplifiers to ADCs and DACs	276
13.3 DAQs powering and grounding.....	277
13.4 Printed circuit design	281
14. Simulation of electronic circuits	284
14.1 Overview of typical simulation programs.....	284
14.2 Program MULTISIM.....	284
14.3 Examples of circuit properties simulations	285
14.3.1 Non-inverting voltage amplifier.....	286
14.3.2 Inverting current amplifier	288
14.3.3 Differential amplifier	289
14.3.4 Instrumentation amplifier.....	290
14.3.5 Pt sensor amplifiers	291
14.3.6 Impedance sensor amplifiers	294
14.3.7 Logarithmic amplifiers	296
14.3.8 Exponential amplifiers.....	298
14.3.9 Operational rectifier	300
14.3.10 Logarithmic RMS converter.....	302
14.3.11 Second order low-pass active filters.....	303
14.3.12 Second order high pass active filters	305
14.3.13 Second order band pass active filters	306
14.3.14 Second order band stop active filters	307
14.3.15 Delta sigma modulator.....	308
14.3.16 Analogue signal digitization and reconstruction.....	310
List of symbols	315
References	317