

# CONTENTS

<b>CONTENTS</b>	4
<b>6. DIGITAL CONTROL</b>	7
6.1. INTRODUCTION	7
6.2. DIGITAL FEEDBACK CONTROL	7
6.3. IDEAL PID CONTROLLERS	9
6.4. REAL PID CONTROLLERS	10
6.5. PID CONTROL LAW FOR AUTOTUNING ALGORITHMS	11
6.6. PID CONTROLLER SETTINGS	12
6.7. PARAMETERS OF INDUSTRIAL PID CONTROLLERS	12
6.8. MICROPROCESSOR-BASED PID CONTROLLER PC96.P	14
6.8.1. General description	14
6.8.2. Connections	15
6.8.3. Features	15
6.8.4. Front panel functions	16
6.8.5. Installation	17
6.8.6. First level parameter programming instructions	17
6.8.7. Second level parameter programming instructions	18
6.8.8. Parameters description	19
6.8.9. Malfunctions signalling	24
6.9. ZEPADIG 10 CONTROLLER	25
6.9.1. Application	25
6.9.2. Operation principle	25
6.9.3. Function description	26
6.9.4. Device control	34
<b>7. LOGIC CONTROL</b>	36
7.1. PLC PROGRAMMING AND HARDWARE FUNDAMENTALS	36
7.1.1. Introduction	36
7.1.2. The PLC's internal organisation program	37
7.1.3. Programming devices for PLCs	37
7.1.4. Data area structure	38
7.2. PLC PROGRAMMING CONCEPTS	40
7.2.1. PLC programming languages	40
7.2.2. Ladder diagram circuit presentation	41
7.2.3. Programming examples	42
7.2.4. Programming bracket-enclosed Boolean equations	44
7.2.5. Connecting "AND" blocks with logic "OR" using "OR LD"	45
7.2.6. Connecting "OR" blocks with logic "AND" using "AND LD"	46
7.2.7. END instruction	46
7.2.8. PLC programming	46

<b>7.3. PROGRAMMING BASIC LOGIC FUNCTIONS</b>	<b>47</b>
7.3.1. "YES" function ( <i>Identity</i> )	47
7.3.2. "NOT" function ( <i>Negation</i> )	47
7.3.3. "AND" function ( <i>Conjunction</i> )	48
7.3.4. "OR" function ( <i>Disjunction</i> )	48
7.3.5. "INHIBITION" function ( <i>Impedance</i> )	48
7.3.6. "EXCLUSIVE OR" function ( <i>Antivalence</i> )	49
7.3.7. "NAND" function ( <i>Exclusion</i> )	49
7.3.8. "NOR" function ( <i>Rejection</i> )	49
7.3.9. "INHIBITED AND" function ( <i>Nonjunction</i> )	50
7.3.10. "INHIBITED OR" function ( <i>Nisjunction</i> )	50
<b>7.4. PLC BISTABLE AND MONOSTABLE OUTPUT RELAYS</b>	<b>51</b>
7.4.1. <i>RS flip-flop output relays</i>	51
7.4.2. <i>KEEP function</i>	52
7.4.3. <i>Latching relays</i>	53
7.4.4. <i>T flip-flop output relays</i>	53
7.4.5. <i>JK flip-flop output relays</i>	54
7.4.6. <i>D flip-flop output relays</i>	55
7.4.7. <i>Miscellaneous internal outputs</i>	56
<b>7.5. TIMERS AND COUNTERS IN PLCs</b>	<b>56</b>
7.5.1. <i>Timer concept</i>	56
7.5.2. <i>Timer programming instructions</i>	57
7.5.3. " <i>ON</i> " - <i>DELAY</i> and " <i>OFF</i> " - <i>DELAY</i> timers	59
7.5.4. <i>Timers and PLC power failure</i>	60
7.5.5. <i>Cascading timers for extra-long time</i>	60
7.5.6. <i>High-speed timers</i>	61
7.5.7. <i>Differentiation function (edge-pulse timer)</i>	61
7.5.8. <i>Counter concept</i>	63
7.5.9. <i>Retentive timers</i>	65
7.5.10. <i>Extra-long timers</i>	65
7.5.11. <i>Cascaded counters</i>	66
7.5.12. <i>Reversible counters</i>	67
7.5.13. <i>Application examples</i>	68
<b>7.6. BUILDING BLOCKS FOR PLC PROGRAMMING</b>	<b>71</b>
7.6.1. <i>A before B circuit</i>	71
7.6.2. <i>One-shot signal</i>	72
7.6.3. <i>Variable flicker signal blocks</i>	73
7.6.4. <i>ON/OFF DELAY block</i>	74
7.6.5. <i>Shift register</i>	74
7.6.6. <i>Multiple word shift register</i>	76
7.6.7. <i>Simultaneous event signalling block</i>	76
7.6.8. <i>Automatic actuator reversal circuit block</i>	77
7.6.9. <i>Building blocks application circuits</i>	78
<b>7.7. SEQUENTIAL TASKS DESIGN</b>	<b>80</b>
7.7.1. <i>Step-action diagram</i>	81
7.7.2. <i>Methods for sequential circuit design</i>	83
7.7.3. <i>Step-counter algorithms for sequential circuit design</i>	84

<b>8. FUZZY LOGIC CONTROL</b>	<b>87</b>
<b>8.1. INTRODUCTION TO FUZZY LOGIC</b>	<b>87</b>
<b>8.2. FUZZY LOGIC IN THE C200H - FZ001</b>	<b>91</b>
<b>8.3. DEVELOPING THE KNOWLEDGE BASE</b>	<b>94</b>
<b>8.4. FUZZY LOGIC - EXAMPLES</b>	<b>99</b>
<b>8.4.1. Example 1 - Pressure and temperature control using fuzzy logic</b>	<b>99</b>
<b>8.4.2. Example 2 - Intelligent vehicle active suspension control system</b>	<b>102</b>
<b>8.4.3. Example 3 - Fuzzy rule-based DC motor speed control</b>	<b>105</b>
<b>8.4.4. Example 4 - Conveyor belt control system</b>	<b>109</b>
<b>LITERATURE</b>	<b>114</b>