

1	NATURE OF ELECTRIC CURRENT .....	1
1.1	ELECTRIC CHARGE, CURRENT AND VOLTAGE .....	1
1.2	RESISTANCE AND CONDUCTIVITY .....	2
1.3	DIRECT AND ALTERNATING CURRENT .....	3
1.4	HARMONIC WAVES .....	5
1.5	AVERAGE AND RMS VALUES .....	7
1.6	ADDITIONAL NOTES .....	8
2	ELECTRICAL APPLIANCES .....	11
2.1	RESISTANCE, INDUCTANCE AND CAPACITANCE .....	11
2.2	ELECTRIC CIRCUIT COMPOSED FROM MORE PARTS .....	14
2.3	PHYSIOLOGICAL EFFECTS AND INJURIES BY ELECTRIC CURRENT .....	18
2.4	ADDITIONAL NOTES .....	19
3	ELECTRIC ENERGY DISTRIBUTION .....	21
3.1	POWER AND ENERGY .....	21
3.2	THREE PHASE SYSTEM .....	22
3.3	ACTIVE POWER ALLOCATION AND DEVICE EFFICIENCY .....	26
3.4	VOLTAGE LEVELS IN THE DISTRIBUTION NETWORK .....	27
3.5	DISTRIBUTION NETWORK .....	29
3.6	ADDITIONAL NOTES .....	30
4	INDUSTRIAL PRODUCTION OF ELECTRIC ENERGY .....	33
4.1	ELECTROMOTIVE FORCE AND TERMINAL VOLTAGE .....	33
4.2	ELECTROMAGNETIC INDUCTION .....	35
4.3	ROTATING GENERATORS .....	37
4.4	THERMAL POWER STATIONS .....	39
4.5	WATER POWER STATIONS .....	41
4.6	TRANSFORMERS .....	42
4.7	ADDITIONAL NOTES .....	44
5	CHEMICAL AND RENEWABLE ENERGY SOURCES .....	45
5.1	CHEMICAL CELLS .....	45
5.2	FUEL CELLS .....	48
5.3	SOLAR CELLS .....	49
5.4	SOME OTHER KINDS OF SOURCES .....	51
5.5	ADDITIONAL NOTES .....	53
6	ELECTRIC SIGNAL AS A CARRIER OF INFORMATION .....	55
6.1	EXPRESSION OF INFORMATION BY VOLTAGE AND CURRENT .....	55
6.2	RELATION BETWEEN ANALOGUE AND DIGITAL EXPRESSION .....	56
6.3	ELECTRONIC DATA .....	58
6.4	INPUT AND OUTPUT DEVICES .....	60
6.5	ADDITIONAL NOTES .....	62
7	SIGNAL TRANSMISSION .....	63
7.1	CABLE LINES .....	63
7.2	WIRELESS TRANSMISSION .....	65
7.3	FREQUENCY BANDS .....	67
7.4	ANTENNAS .....	68
7.5	DATA TRANSMISSION .....	69
7.6	ADDITIONAL NOTES .....	71
8	LOGICAL CONTROL CIRCUITS OF ELECTRIC DEVICES .....	73
8.1	POWER AND CONTROL CIRCUITS .....	73
8.2	LOGICAL CIRCUITS .....	74
8.3	CONTROLLERS .....	77
8.4	ACTION UNITS .....	79
8.5	ADDITIONAL NOTES .....	80

9	ELECTROMECHANICAL EQUIPMENTS.....	83
9.1	THE FORCE CAUSED BY MAGNETIC FIELD .....	83
9.2	ELECTROMAGNETS .....	84
9.3	TORQUE .....	86
9.4	DC MOTOR.....	87
9.5	THREE PHASE AC ROTATING MACHINES.....	89
9.6	ADDITIONAL NOTES.....	92
10	ELECTRIC ENERGY CONVERTORS.....	93
10.1	POWER SEMICONDUCTOR DEVICES.....	93
10.2	SEMICONDUCTOR RECTIFIERS .....	95
10.3	ANOTHER TYPES OF SEMICONDUCTOR CONVERTERS .....	99
10.4	ADDITIONAL NOTES .....	100
11	CONTROL OF ELECTRIC EQUIPMENT BEHAVIOUR .....	103
11.1	THE ROLE OF A CONTROLLER .....	103
11.2	CONTROL LOOPS .....	104
11.3	CONTINUOUS CONTROLLER TYPES .....	106
11.4	CONTROLLER ADJUSTEMENT.....	108
11.5	ADDITIONAL NOTES.....	110
12	MATERIALS FOR ELECTRIC EQUIPMENT .....	111
12.1	INSULANTS .....	111
12.2	SEMICONDUCTORS .....	112
12.3	CONDUCTORS.....	113
12.4	MAGNETIC CIRCUITS .....	115
12.5	MAGNETIC MATERIALS.....	117
12.6	CONSTRUCTIONAL MATERIALS.....	120
12.7	ADDITIONAL NOTES.....	121
13	TECHNICAL REQUIREMENTS ON PRODUCTS.....	123
13.1	TECHNICAL STANDARDIZATION .....	123
13.2	ELECTRIC EQUIPMENT AND ECOLOGY .....	126
13.3	THE LAW ABOUT TECHNICAL REQUIREMENTS ON PRODUCTS.....	127
13.4	ADDITIONAL NOTES.....	129
14	GETTING STARTED WITH LABORATORY SYSTEM RC2000.....	131
14.1	SYSTEM MODULES.....	131
14.2	PC MEASURING UNIT - ADDU.....	136
14.3	PROGRAM „TWO CHANNEL OSCILLOSCOPE“.....	137
15	EXPERIMENTS WITH LABORATORY SYSTEM RC2000.....	143
15.1	AC POWER SUPPLY WITH RESISTIVE LOAD .....	143
15.2	AC POWER SUPPLY WITH INDUCTIVE LOAD .....	145
15.3	AC POWER SUPPLY WITH CAPACITIVE LOAD .....	147
15.4	MEASUREMENT OF AC ACTIVE POWER P .....	149
15.5	SERIAL RLC CIRCUIT – RESONANCE EFFECT.....	151
15.6	1-PHASE NON CONTROLLED SINGLE PULSE RECTIFIER – RL LOAD .....	152
15.7	1-PHASE NON CONTROLLED SINGLE PULSE RECTIFIER – RC LOAD.....	154
15.8	SERIAL RC CIRCUIT – TRANSIENT PROCESS .....	155
15.9	SERIAL RL CIRCUIT – TRANSIENT PROCESS .....	157
15.10	SERIAL RLC CIRCUIT – TRANSIENT PROCESS .....	159
15.11	1-PHASE 1-PULSE CONTROLLED RECTIFIER – INTERFERENCE.....	161
15.12	MODEL OF CONTROLLED MEMBER – TIME CONSTANT .....	163
15.13	SYSTEM WITH P-CONTROLLER – VARIATION OF $K_p$ .....	165
15.14	SYSTEM WITH I-CONTROLLER – VARIATION OF $T_i$ .....	167

CONTROLLERS 83  
 ACTIVE FILTERS 84  
 ADDITIONAL NOTES 86