

# T A B L E O F C O N T E N T S

Preface .....	xxi
Glossary of Symbols.....	xxvii
<b>1 Fundamentals.....</b>	<b>1</b>
1.1 Impedance of Linear, Time-Invariant, Lumped-Element Circuits.....	1
1.2 Power Ratios .....	2
1.3 Rules of Scaling .....	5
1.3.1 Scaling of Physical Size .....	6
1.3.1.1 Scaling Inductors.....	8
1.3.1.2 Scaling Transmission-Line Dimensions.....	8
1.3.2 Power Scaling .....	9
1.3.3 Time Scaling .....	10
1.3.4 Impedance Scaling with Constant Voltage .....	12
1.3.5 Dielectric-Constant Scaling .....	14
1.3.5.1 Partially Embedded Transmission Lines.....	15
1.3.6 Magnetic Permeability Scaling .....	15
1.4 The Concept of Resonance .....	16
1.5 Extra for Experts: Maximal Linear System Response to a Digital Input .....	22
<b>2 Transmission Line Parameters.....</b>	<b>29</b>
2.1 Telegrapher's Equations .....	31
2.1.1 <i>So Good It Works on Barbed Wire</i> .....	34
2.1.2 The No-Storage Principle and Its Implications for Returning Signal Current .....	35
2.2 Derivation of Telegrapher's Equations .....	38
2.2.1 Definition of Characteristic Impedance $Z_C$ .....	39
2.2.2 Changes in Characteristic Impedance .....	40
2.2.3 Calculation of Impedance $Z_C$ From Parameters $R$ , $L$ , $G$ , And $C$ .....	41
2.2.4 Definition of Propagation Coefficient $\gamma$ .....	44
2.2.5 Calculation of Propagation Coefficient $\gamma$ from Parameters $R$ , $L$ , $G$ , and $C$ ... 46	46
2.3 Ideal Transmission Line.....	48
2.4 DC Resistance.....	55
2.5 DC Conductance .....	57

2.6	Skin Effect .....	58
2.6.1	What Causes the Skin Effect, and What Does It Have to Do With Skin?.....	58
2.6.2	Eddy Currents within a Conductor.....	61
2.6.3	High and Low-Frequency Approximations for Series Resistance .....	63
2.7	Skin-Effect Inductance.....	66
2.8	Modeling Internal Impedance .....	67
2.8.1	Practical Modeling of Internal Impedance .....	70
2.8.2	Special Issues Concerning Rectangular Conductors .....	73
2.9	Concentric-Ring Skin-Effect Model .....	75
2.9.1	<i>Modeling Skin Effect</i> .....	76
2.9.2	<i>Regarding Modeling Skin Effect</i> .....	79
2.10	Proximity Effect.....	79
2.10.1	Proximity Factor .....	81
2.10.2	Proximity Effect for Coaxial Cables .....	84
2.10.3	Proximity Effect for Microstrip and Stripline Circuits.....	85
2.10.4	Last Words on Proximity Effect .....	85
2.10.4.1	<i>Proximity Effect II</i> .....	85
2.10.4.2	<i>2-D Quasistatic Field Solvers</i> .....	87
2.11	Surface Roughness.....	90
2.11.1	Severity of Surface Roughness .....	90
2.11.2	Onset of Roughness Effect.....	91
2.11.3	Roughness of Pcb Materials.....	91
2.11.4	Controlling Roughness.....	92
2.12	Dielectric Effects .....	94
2.12.1	Dielectric Loss Tangent .....	98
2.12.2	Rule of Mixtures .....	99
2.12.3	Calculating the Loss Tangent for a Uniform Dielectric Mixture .....	101
2.12.4	Calculating the Loss Tangent When You Don't Know $q$ .....	103
2.12.5	Causality and the Network Function Relations.....	105
2.12.6	Finding $ er $ to Match a Measured Loss Tangent .....	110
2.12.7	Kramers-Kronig Relations .....	114
2.12.8	Complex Magnetic Permeability.....	115
2.13	Impedance in Series with the Return Path .....	115
2.14	Slow-Wave Mode On-Chip .....	117
	<b>Performance Regions.....</b>	<b>121</b>
3.1	Signal Propagation Model.....	121
3.1.1	Extracting Parameters for RLGC Simulators.....	127
3.2	Hierarchy of Regions .....	128
3.2.1	<i>A Transmission Line Is Always a Transmission Line</i> .....	130
3.3	Necessary Mathematics: Input Impedance and Transfer Function .....	132
3.4	Lumped-Element Region .....	135
3.4.1	Boundary of Lumped-Element Region .....	136
3.4.2	Pi Model.....	137

3.4.3	Taylor-Series Approximation of H (Lumped-Element Region).....	139
3.4.4	Input impedance (Lumped-Element Region).....	140
3.4.5	Transfer Function (Lumped-Element Region).....	143
3.4.6	Step Response (Lumped-Element Region) .....	145
3.5	RC Region.....	148
3.5.1	Boundary of RC Region.....	149
3.5.2	Input Impedance (RC Region) .....	151
3.5.3	Characteristic Impedance (RC Region).....	152
3.5.4	General Behavior within RC Region .....	153
3.5.5	Propagation Coefficient (RC Region).....	155
3.5.6	Transfer Function (RC Region) .....	155
3.5.6.1	Propagation Function of RC Line with Open-Circuited Load .....	155
3.5.6.2	Propagation Function of RC Line with Matched End Termination .....	156
3.5.6.3	Propagation Function of RC Line with Matched Source Termination....	156
3.5.6.4	Propagation Function of RC Line with Resistive End Termination.....	157
3.5.7	Normalized Step Response (RC Region).....	157
3.5.8	Tradeoffs Between Distance and Speed (RC Region) .....	159
3.5.9	Closed-Form Solution for Step Response (RC Region).....	159
3.5.10	Elmore Delay Estimation (RC Region).....	160
3.6	LC Region (Constant-Loss Region).....	166
3.6.1	Boundary of LC Region.....	166
3.6.2	Characteristic Impedance (LC Region).....	167
3.6.3	Influence of Series Resistance on TDR Measurements .....	169
3.6.4	Propagation Coefficient (LC Region) .....	173
3.6.5	Possibility of Severe Resonance within the LC Region.....	176
3.6.5.1	Alternate Interpretation of Equation [3.17].....	178
3.6.5.2	Practical Effect of Resonance .....	179
3.6.6	Terminating an LC Transmission Line .....	179
3.6.6.1	End Termination .....	180
3.6.6.2	Source Termination.....	181
3.6.6.3	Both-Ends Termination.....	181
3.6.6.4	Subtle Differences Between Termination Styles.....	181
3.6.6.5	Application of Termination Equations to Other Regions.....	183
3.6.7	Tradeoffs Between Distance And Speed (LC Region).....	183
3.6.8	Mixed-Mode Operation (LC and RC Regions).....	184
3.7	Skin-Effect Region.....	185
3.7.1	Boundary of Skin-Effect Region.....	185
3.7.2	Characteristic Impedance (Skin-Effect Region).....	186
3.7.3	Influence of Skin-Effect on TDR Measurement .....	188
3.7.4	Propagation Coefficient (Skin-Effect Region).....	189
3.7.5	Possibility of Severe Resonance within Skin-Effect Region.....	193
3.7.5.1	Subtle Differences Between Termination Styles.....	194
3.7.5.2	Application of Termination Equations to Other Regions.....	194
3.7.6	Step Response (Skin-Effect Region).....	195

3.7.7	Tradeoffs Between Distance and Speed (Skin-Effect Region)	199
3.8	Dielectric Loss Region	200
3.8.1	Boundary of Dielectric-Loss-Limited Region	200
3.8.2	Characteristic Impedance (Dielectric-Loss-Limited Region)	202
3.8.3	Influence of Dielectric Loss on TDR Measurement	205
3.8.4	Propagation Coefficient (Dielectric-Loss-Limited Region)	206
3.8.5	Possibility of Severe Resonance within Dielectric-Loss Limited Region	210
3.8.5.1	Subtle Differences Between Termination Styles	211
3.8.5.2	Application of Termination Equations to Other Regions	211
3.8.6	Step Response (Dielectric-Loss-Limited Region)	212
3.8.7	Tradeoffs Between Distance and Speed (Dielectric-Loss Region)	216
3.9	Waveguide Dispersion Region	216
3.9.1	Boundary of Waveguide-Dispersion Region	217
3.10	Summary of Breakpoints Between Regions	218
3.11	Equivalence Principle for Transmission Media	221
3.12	Scaling Copper Transmission Media	224
3.13	Scaling Multimode Fiber-Optic Cables	229
3.14	Linear Equalization: Long Backplane Trace Example	230
3.15	Adaptive Equalization: Accelerant Networks Transceiver	234
	<b>Frequency-Domain Modeling</b>	<b>237</b>
1	Going Nonlinear	237
2	Approximations to the Fourier Transform	239
3	Discrete Time Mapping	241
4	Other Limitations of the FFT	243
5	Normalizing the Output of an FFT Routine	243
4.5.1	Deriving the DFT Normalization Factors	244
5	Useful Fourier Transform-Pairs	245
7	Effect of Inadequate Sampling Rate	247
3	Implementation of Frequency-Domain Simulation	249
0	Embellishments	251
4.9.1	What if a Large Bulk-Transport Delay Causes the Waveform to Slide Off the end of the Time-Domain Window?	251
4.9.2	How Do I Transform an Arbitrary Data Sequence?	251
4.9.3	How Do I Shift the Time-Domain Waveforms?	252
4.9.4	What If I Want to Model a More Complicated System?	252
4.9.5	What About Differential Modeling?	252
0	Checking the Output of Your FFT Routine	253
	<b>Pcb (printed-circuit board) Traces</b>	<b>255</b>
	Pcb Signal Propagation	257
5.1.1	Characteristic Impedance and Delay	257
5.1.2	Resistive Effects	258
5.1.2.1	DC Resistance of Pcb Trace	258

5.1.2.2	AC Resistance of Pcb Trace	258
5.1.2.3	Calculation of Perimeter of Pcb Trace	261
5.1.2.4	Very Low Impedance Pcb Trace	262
5.1.2.5	Calculation of Skin-Effect Loss Coefficient for Pcb trace	262
5.1.2.6	<i>Popsicle-Stick Analysis</i>	262
5.1.2.7	<i>Nickel-Plated Traces</i>	266
5.1.3	Dielectric Effects	268
5.1.3.1	Estimating the Effective Dielectric Constant for a Microstrip	269
5.1.3.2	Propagation Velocity	270
5.1.3.3	Calculating the Effective Loss Tangent for a Microstrip	270
5.1.3.4	Dielectric Properties of Laminate Materials (core and prepreg)	271
5.1.3.5	<i>Variations in Dielectric Properties with Temperature</i>	275
5.1.3.6	Passivation and Soldermask	277
5.1.3.7	Dielectric Properties of Soldermask Materials	280
5.1.3.8	Calculation of Dielectric Loss Coefficient for Pcb Trace	280
5.1.4	Mixtures of Skin Effect and Dielectric Loss	281
5.1.5	Non-TEM Modes	282
5.1.5.1	<i>Strange Microstrip Modes</i>	282
5.1.5.2	Simulation of Non-TEM Behavior	286
5.2	Limits to Attainable Distance	288
5.2.1	<i>SONET Data Coding</i>	291
5.3	Pcb Noise and Interference	294
5.3.1	Pcb: Reflections	294
5.3.1.1	<i>Both Ends Termination</i>	295
5.3.1.2	Pcb: Lumped-Element Reflections	297
5.3.1.3	<i>Potholes</i>	300
5.3.1.4	Inductive Potholes	303
5.3.1.5	<i>Who's Afraid of the Big, Bad Bend?</i>	304
5.3.1.6	<i>Stubs and Vias</i>	305
5.3.1.7	<i>Parasitic Pads</i>	306
5.3.1.8	<i>How Close Is Close Enough?</i>	309
5.3.1.9	<i>Placement of End Termination</i>	312
5.3.1.10	<i>Making an Accurate Series Termination</i>	314
5.3.1.11	<i>Matching Pads</i>	315
5.3.2	Pcb Crosstalk	318
5.3.2.1	Purpose of Solid Plane Layers	318
5.3.2.2	Variations with Trace Geometry	318
5.3.2.3	Directionality	319
5.3.2.4	NEXT: Near-End or Reverse Crosstalk	320
5.3.2.5	FEXT: Far-End or Forward Crosstalk	321
5.3.2.6	Special Considerations	322
5.3.2.7	<i>Directionality of Crosstalk</i>	323
5.4	Pcb Connectors	326
5.4.1	<i>Mutual Understanding</i>	326

5.4.2	Through-Hole Clearances.....	328
5.4.3	Measuring Connectors.....	330
5.4.4	Tapered Transitions.....	332
5.4.5	Straddle-Mount Connectors.....	335
5.4.6	Cable Shield Grounding.....	336
	Modeling Vias.....	338
5.5.1	Incremental Parameters of a Via.....	338
5.5.2	Three Models for a Via.....	341
5.5.3	Dangling Vias.....	343
5.5.4	Capacitance Data.....	345
5.5.4.1	Three-Layer Via Capacitance.....	345
5.5.4.2	Effect of Back-Drilling.....	346
5.5.4.3	Effect of Multiple Planes.....	347
5.5.5	Inductance Data.....	351
5.5.5.1	Through-Hole Via Inductance.....	351
5.5.5.2	Via Crosstalk.....	354
	<i>The Future of On-Chip Interconnections</i> .....	359
	<b>Differential Signaling.....</b>	<b>363</b>
	Single-Ended Circuits.....	363
	Two-Wire Circuits.....	368
	Differential Signaling.....	370
	Differential and Common-Mode Voltages and Currents.....	374
	Differential and Common-Mode velocity.....	376
	Common-Mode Balance.....	377
	Common-Mode Range.....	378
	Differential to Common-Mode Conversion.....	378
	Differential Impedance.....	380
9.1	Relation Between Odd-Mode and Uncoupled Impedance.....	383
9.2	Why the Odd-Mode Impedance Is Always Less Than the Uncoupled Impedance.....	383
9.3	<i>Differential Reflections</i> .....	384
	Pcb Configurations.....	385
10.1	<i>Differential (Microstrip) Trace Impedance</i> .....	386
10.2	Edge-Coupled Stripline.....	389
10.3	<i>Breaking Up a Pair</i> .....	397
10.4	Broadside-Coupled Stripline.....	399
	Pcb Applications.....	404
11.1	Matching to an External, Balanced Differential Transmission Medium.....	404
11.2	Defeating ground bounce.....	405
11.3	Reducing EMI with Differential Signaling.....	405
11.4	Punching Through a Noisy Connector.....	407
6.11.4.1	<i>Differential Signaling (Through Connectors)</i> .....	408
11.5	Reducing Clock Skew.....	409

6.11.6	Reducing Local Crosstalk.....	411
6.11.7	A Good Reference about Transmission Lines.....	413
6.11.8	<i>Differential Clocks</i> .....	413
6.11.9	<i>Differential Termination</i> .....	414
6.11.10	<i>Differential U-Turn</i> .....	417
6.11.11	<i>Your Layout Is Skewed</i> .....	419
6.11.12	<i>Buying Time</i> .....	420
6.12	Intercabinet Applications.....	422
6.12.1	Ribbon-Style Twisted-Pair Cables.....	423
6.12.2	Immunity to Large Ground Shifts.....	424
6.12.3	Rejection of External Radio-Frequency Interference (RFI).....	426
6.12.4	Differential Receivers Have Superior Tolerance to Skin Effect and Other High-Frequency Losses.....	427
6.13	LVDS Signaling.....	429
6.13.1	Output Levels.....	429
6.13.2	Common-Mode Output.....	430
6.13.3	Common-Mode Noise Tolerance.....	430
6.13.4	Differential-Mode Noise Tolerance.....	431
6.13.5	Hysteresis.....	431
6.13.6	Impedance Control.....	432
6.13.7	Trace Radiation.....	435
6.13.8	Risetime.....	435
6.13.9	Input Capacitance.....	435
6.13.10	Skew.....	435
6.13.11	Fail-Safe.....	436
<b>7</b>	<b>Generic Building-Cabling Standards.....</b>	<b>439</b>
7.1	Generic Cabling Architecture.....	442
7.2	SNR Budgeting.....	446
7.3	Glossary of Cabling Terms.....	446
7.4	Preferred Cable Combinations.....	449
7.5	FAQ: Building-Cabling Practices.....	449
7.6	Crossover Wiring.....	451
7.7	Plenum-Rated Cables.....	452
7.8	Laying cables in an Uncooled Attic Space.....	453
7.9	FAQ: Older Cable Types.....	453
<b>8</b>	<b>100-Ohm Balanced Twisted-Pair Cabling.....</b>	<b>457</b>
8.1	UTP Signal Propagation.....	459
8.1.1	UTP Modeling.....	460
8.1.2	Adapting the Metallic-Transmission Model.....	462
8.2	UTP Transmission Example: 10BASE-T.....	465
8.3	UTP Noise and Interference.....	471
8.3.1	UTP: Far-End Reflections.....	471

Table of Contents

2 UTP: Near-End Reflections ..... 475

3.3.2.1 UTP: (Structural) Return Loss ..... 477

3.3.2.2 Modeling Structural Return Loss ..... 480

3 UTP: Hybrid Circuits ..... 481

4 UTP: Near-End Crosstalk ..... 487

5 UTP: Alien crosstalk ..... 490

6 UTP: Far-End Crosstalk ..... 490

7 Power sum NEXT and ELFEXT ..... 493

8 UTP: Radio-Frequency Interference ..... 493

9 UTP: Radiation ..... 496

UTP Connectors ..... 497

Issues with Screening ..... 501

Category-3 UTP at Elevated Temperature ..... 502

**150-Ohm STP-A Cabling ..... 505**

150-Ω STP-A Signal Propagation ..... 506

150-Ω STP-A Noise and Interference ..... 506

150-Ω STP-A: Skew ..... 507

150-Ω STP-A: Radiation and Safety ..... 508

150-Ω STP-A: Comparison with UTP ..... 509

150-Ω STP-A Connectors ..... 509

**Coaxial Cabling ..... 513**

Coaxial Signal Propagation ..... 515

1.1 Stranded Center-Conductors ..... 522

1.2 *Why 50 Ohms?* ..... 523

1.3 *50-Ohm Mailbag* ..... 526

Coaxial Cable Noise and Interference ..... 528

2.1 Coax: Far-End Reflected Noise ..... 528

2.2 Coax: Radio Frequency Interference ..... 529

2.3 Coax: Radiation ..... 529

2.4 Coaxial Cable: Safety Issues ..... 530

Coaxial Cable Connectors ..... 532

**Fiber-Optic Cabling ..... 537**

Making Glass Fiber ..... 538

Finished Core Specifications ..... 539

Cabling the Fiber ..... 541

Wavelengths of Operation ..... 543

Multimode Glass Fiber-Optic Cabling ..... 544

1 Multimode Signal Propagation ..... 546

2 Why Is Graded-Index Fiber Better than Step-Index? ..... 551

3 Standards for Multimode Fiber ..... 552

4 What Considerations Govern the Use of 50-micron Fiber? ..... 554

Table of Contents

11.5.5 Multimode Optical Performance Budget ..... 555

11.5.5.1 Multimode Dispersion Budget ..... 555

11.5.5.2 Multimode Attenuation Budget ..... 566

11.5.6 Jitter ..... 568

11.5.7 Multimode Fiber-Optic Noise and Interference ..... 570

11.5.8 Multimode Fiber Safety ..... 571

11.5.9 Multimode Fiber with Laser Source ..... 571

11.5.10 VCSEL Diodes ..... 573

11.5.11 Multimode Fiber-Optic Connectors ..... 575

11.6 Single-Mode Fiber-Optic Cabling ..... 576

11.6.1 Single-Mode Signal Propagation ..... 577

11.6.2 Single-Mode Fiber-Optic Noise and Interference ..... 578

11.6.3 Single-Mode Fiber Safety ..... 578

11.6.4 Single-Mode Fiber-Optic Connectors ..... 578

**12 Clock Distribution ..... 579**

12.1 *Extra Fries, Please* ..... 582

12.2 Arithmetic of Clock Skew ..... 584

12.3 Clock Repeaters ..... 589

12.3.1 Active Skew Correction ..... 593

12.3.2 Zero-Delay Clock Repeaters ..... 594

12.3.3 Compensating for Line Length ..... 595

12.4 Stripline vs. Microstrip Delay ..... 596

12.5 Importance of Terminating Clock Lines ..... 599

12.6 Effect of Clock Receiver Thresholds ..... 601

12.7 Effect of Split Termination ..... 602

12.8 Intentional Delay Adjustments ..... 605

12.8.1 Fixed Delay ..... 605

12.8.2 Adjustable Delays ..... 607

12.8.3 Automatically Programmable Delays ..... 609

12.8.4 *Serpentine Delays* ..... 610

12.8.5 Switchback Coupling ..... 612

12.9 Driving Multiple Loads with Source Termination ..... 616

12.9.1 *To Tee or Not To Tee* ..... 619

12.9.2 *Driving Two Loads* ..... 625

12.10 Daisy-Chain Clock Distribution ..... 627

12.10.1 Case Study of Daisy-Chained Clock ..... 629

12.11 *The Jitters* ..... 634

12.11.1 When Clock Jitter Matters ..... 636

12.11.1.1 Clock Jitter Rarely Matters within the Boundaries of a Synchronous State Machine ..... 636

12.11.1.2 Clock Jitter Propagation ..... 636

12.11.1.3 Variance of the Tracking Error ..... 640

12.11.1.4 Clock Jitter in FIFO-Based Architectures ..... 643